 


# # SR latch using NOR gate



## # Explanation of the Image: SR Latch using NOR Gate

This image represents an SR (Set-Reset) Latch built using NOR gates. The SR latch is a basic sequential logic circuit used for storing one bit of information. It has two inputs:

- S (Set): Used to set the output  $Q = 1$  (high state).
- R (Reset): Used to reset the output  $Q = 0$  (low state).

The circuit consists of two NOR gates, where:

- The output of each NOR gate is fed back into the other NOR gate as an input.
- The two outputs  $Q$  and  $Q'$  ( $Q$  complement) are always opposite to each other ( $Q' = \text{NOT } Q$ ).

## Working of SR Latch using NOR Gates

### # Case 1: S = 0, R = 0 (No Change / Memory State)

- If both  $S$  and  $R$  are 0, the latch remains in its previous state.
- The stored value does not change.
- $Q$  and  $Q'$  remain in their previous states.

### # Case 2: S = 0, R = 1 (Reset State)

- The upper NOR gate has inputs  $R = 1$  and  $Q'$ , so it outputs  $Q = 0$ .
- The lower NOR gate now has inputs  $S = 0$ ,  $Q = 0$ , so it outputs  $Q' = 1$ .
- The latch is in the reset state ( $Q = 0$ ,  $Q' = 1$ ).

### # Case 3: S = 1, R = 0 (Set State)

- The lower NOR gate has inputs  $S = 1$  and  $Q$ , so it outputs  $Q' = 0$ .
- The upper NOR gate now has inputs  $R = 0$ ,  $Q' = 0$ , so it outputs  $Q = 1$ .
- The latch is in the set state ( $Q = 1$ ,  $Q' = 0$ ).

### # Case 4: S = 1, R = 1 (Invalid / Undefined State)

- Both NOR gates output 0, causing an invalid state.
- This state is not allowed because it makes  $Q$  and  $Q'$  equal, violating the principle of an SR latch.

Truth Table of SR Latch using NOR Gate

S (Set)	R (Reset)	Q (Output)	Q' (Complement)	State
0	0	No Change	No Change	Memory
0	1	0	1	Reset
1	0	1	0	Set
1	1	Invalid	Invalid	Undefined

## Conclusion

The SR Latch using NOR gates is a fundamental sequential circuit that stores one bit of data. It is used in memory units, flip-flops, and other digital logic applications. However, the  $S = 1$ ,  $R = 1$  state is invalid, so additional logic (like an SR latch with enable or a clocked SR flip-flop) is used in practical applications to avoid this issue.